

# DISSIPATION LIMITER

by C. Zschocke

THE secondary alternating voltage in power supplies stabilized with the aid of series regulators is normally calculated to ensure that with maximum output voltage and current the potential across the reservoir capacitor does not drop below the minimum voltage,  $U_r$ , required for satisfactory operation of the regulator. When the supply operates below maximum output voltage and current, the power that is then not required is converted into heat. Moreover, the design allows for maximum output voltage and current even when the mains voltage is at its lowest specified level.

The secondary voltage may well be specified too high, with the result that when the mains voltage is at its highest specified level and the power supply is open-circuited, the maximum permissible potential across the reservoir capacitor, and thus that at the input of the regulator, may easily be exceeded.

It is clear that in most power supplies, the specified voltage levels for the regulator and reservoir capacitor are needlessly high.


## Possible solutions

The uneconomical design outlined above may be improved in several ways. It is, for instance, possible, with the aid of relays, to select secondary alternating voltages according to the load requirement. This is, however, possible only with a very special, and therefore expensive, mains transformer. Another possibility is to use phase gating control. This, however, requires fairly high switching currents and causes noise on the mains supply. Moreover, capacitors that can withstand high current pulses must be used and these are expensive.

A third method is used in the circuit presented here. In this, the charging of the reservoir capacitor is interrupted when a certain potential across the capacitor is reached. The circuit, which can be added to most existing

**Dissipation in electronically regulated power supplies, manifested by heat, is a problem that is normally tackled by providing external heat sinks.**

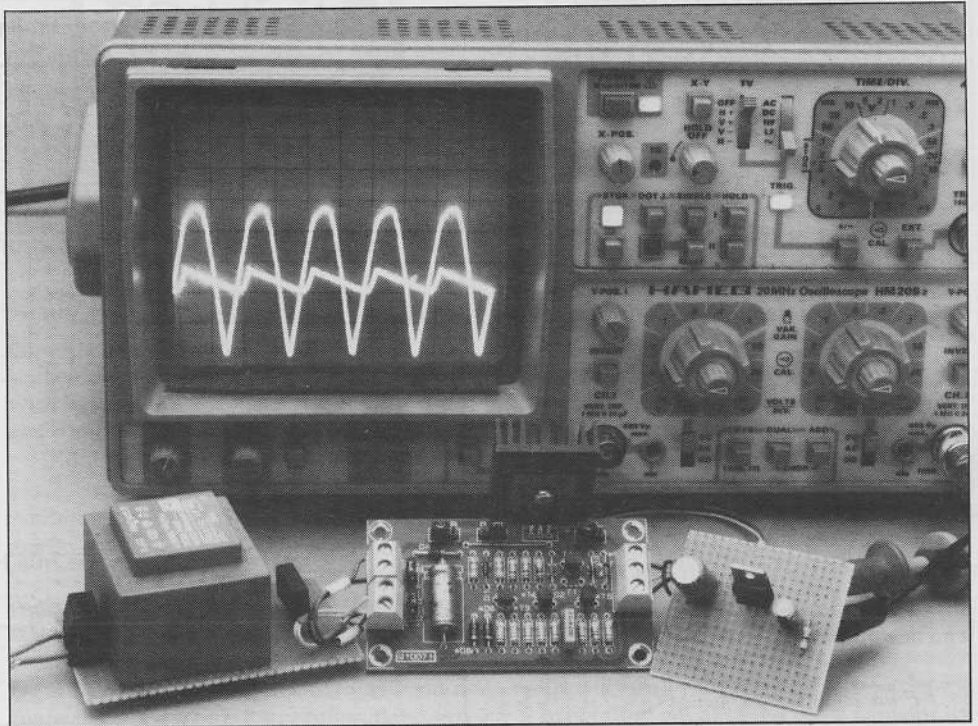**The limiter presented here offers a more intelligent solution. It can be used as an add-on unit with virtually any power supply.**



- regulated mains power supplies,
- minimizes the power dissipation;
  - offers an additional reduction in dissipation during a short-circuit or during current limiting;
  - is inexpensive to build;
  - uses only standard, readily available components;
  - needs only little space;
  - is suitable for high-current supplies;

- can be used with positive and negative series regulators.

## Principle of operation

In Figure 1, an electronic switch, for instance, a SIPMOS transistor, is inserted between the rectifier and the reservoir capacitor. At the start of each half cycle, the switch is on ( $U_r > 3V$ ). A charging current flows into the capacitor

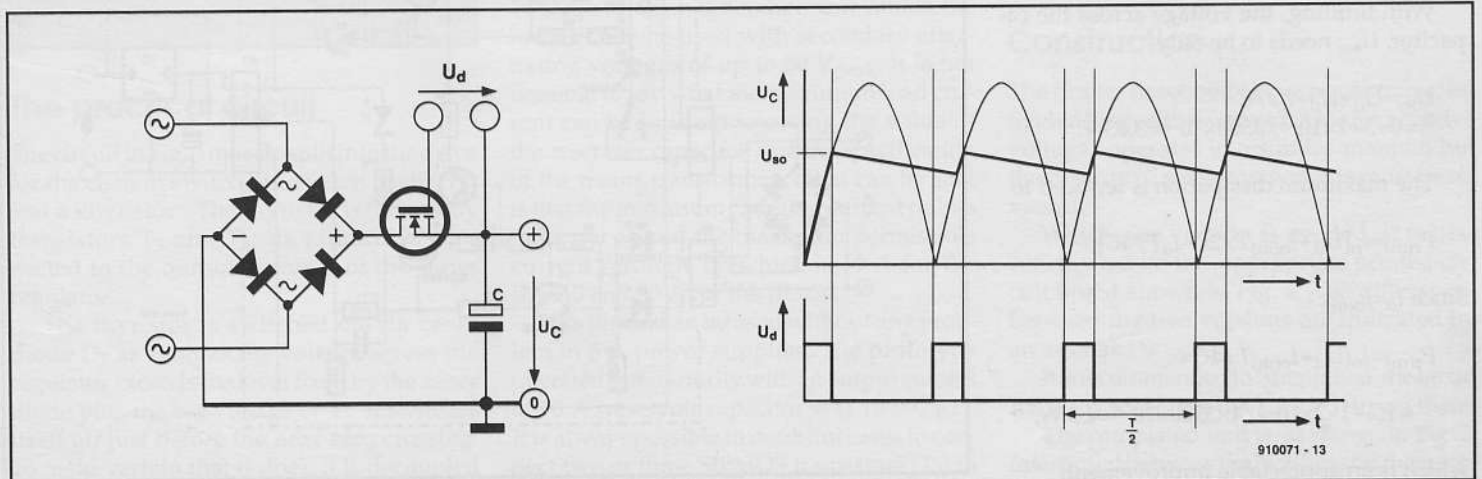


Fig. 1. Principle of operation of the dissipation limiter.

and the potential,  $U_c$ , across the capacitor follows the instantaneous level of the half-wave voltage. When  $U_c$  has reached the minimum level,  $U_{so}$ , required for the wanted output voltage,  $U_o$ , the charging current is switched off until the end of the half cycle. The level of  $U_{so}$  must be chosen to ensure that  $U_c$  does not drop below  $U_r$  until charging current begins to flow again at the start of the next half cycle. This voltage is the sum of the wanted output voltage, the drop across the regulator,  $U_d$ , and the voltage resulting from the discharging of the capacitor. The difference  $\Delta U$  that is, the series switch-off voltage,  $U_{so(m)}$ , between  $U_r$  and  $U_{so}$  is easily determined, since it is directly proportional to the charging current; in fact,  $\Delta U = It / C$ , where  $I$  is the charging current,  $t$  is the time during which charging current flows, and  $C$  is the capacitance of the reservoir capacitor. Thus,

$$U_{so} = U_o + U_d + \Delta U$$

$$= U_o + U_d + It / C.$$

The time  $t$  is, in full-wave rectification, equal to a half cycle of the mains frequency, that is,  $T/2$ . Then,

$$U_{so} = U_o + U_d + IT / 2C.$$

If now the maximum permissible output current,  $I_{o(m)}$  is substituted for  $I$ , the highest potential drop across the regulator (at the start of each half cycle) is

$$U_{so(m)} = U_{so} - U_o = U_d + I_{o(m)}T / 2C.$$

From this, the instantaneous dissipation,  $P_r$ , can be computed:

$$P_r = I_o U_{so(m)} = I_o [U_d + I_{o(m)}T / 2C - I_o T / 4C].$$

As an example: a power supply with a reservoir capacitor of 3300  $\mu F$  is required to provide an output voltage of 0-15 V at a maximum current of 1 A. Since the potential drop across the regulator is 3 V, the voltage across the capacitor,  $U_c$ , must be at least 18 V. Without limiting, the maximum power loss,  $P_{r(m)}$ , in the regulator is  $18 \times 1 = 18$  W (which is, for instance, the case when maximum current flows at very low output voltage as in a short-circuit condition).

With limiting, the voltage across the capacitor,  $U_{so}$ , needs to be only

$$U_{so} = U_o + U_d + I_o t / C =$$

$$= 0 + 3 + 1 \times 10^{-2} / 3300 \times 10^{-6} = 3.03 \text{ V.}$$

The maximum dissipation is reduced to

$$P_{r(m)} = I_o [U_d + I_{o(m)}T / 2C - I_o T / 4C].$$

Since  $I_o = I_{o(m)}$ ,

$$P_{r(m)} = I_o (U_d + I_{o(m)}T / 4C =$$

$$= 1(3 + 1 \times 2 \times 10^{-2} / 4 \times 3300 \times 10^{-6}) = 4.5 \text{ W,}$$

which is an appreciable improvement.

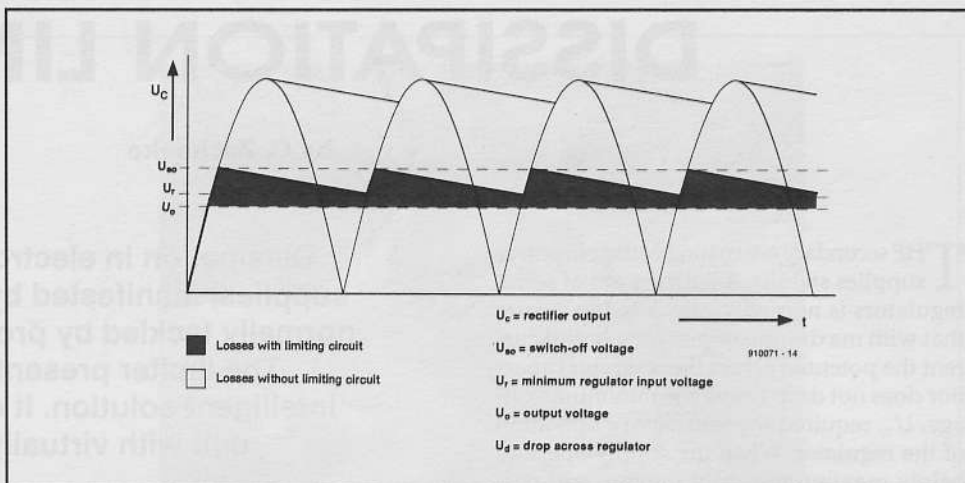


Fig. 2. Dissipation with and without limiter.

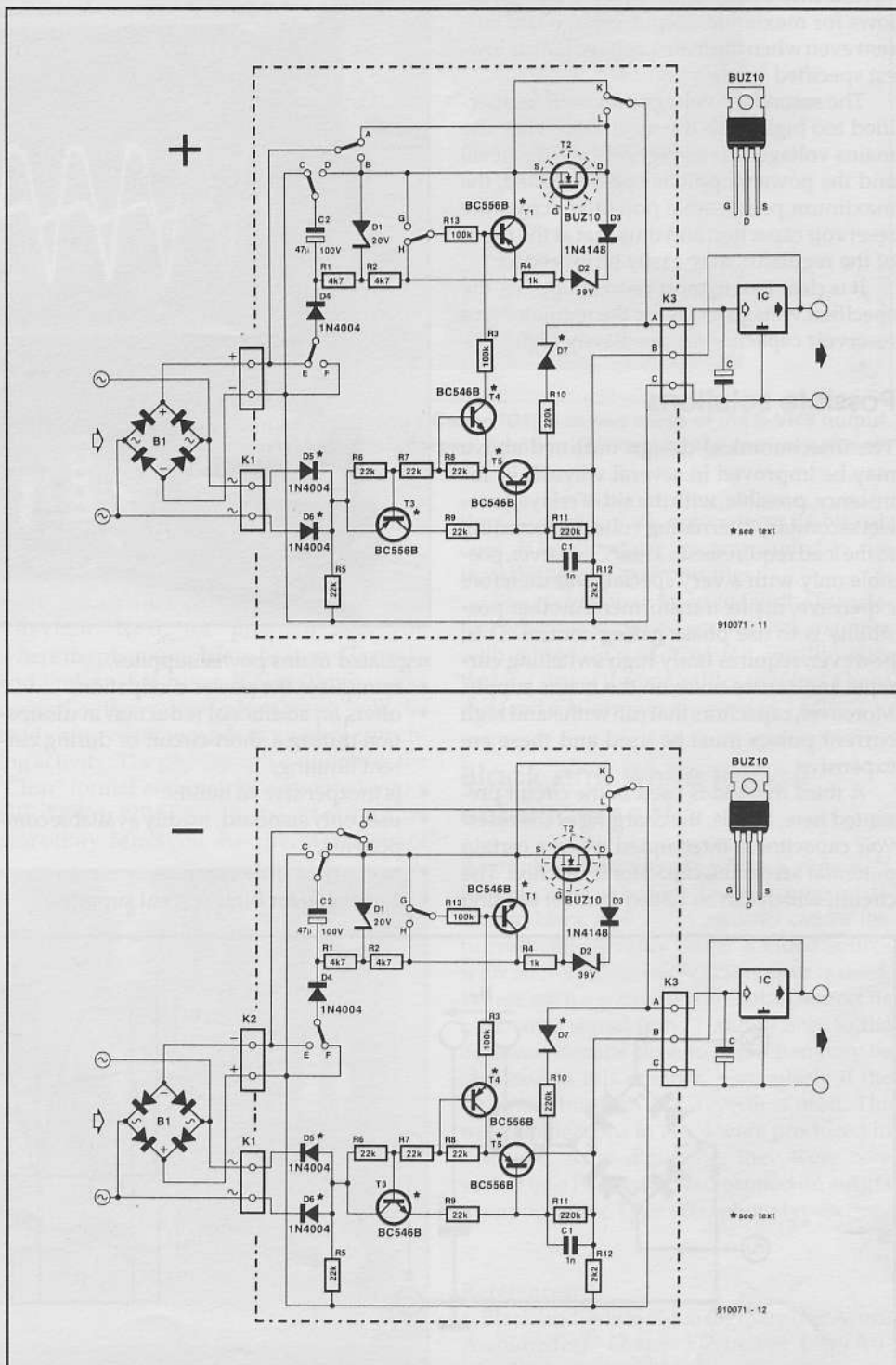


Fig. 3. Circuit diagram for both versions of the dissipation limiter.

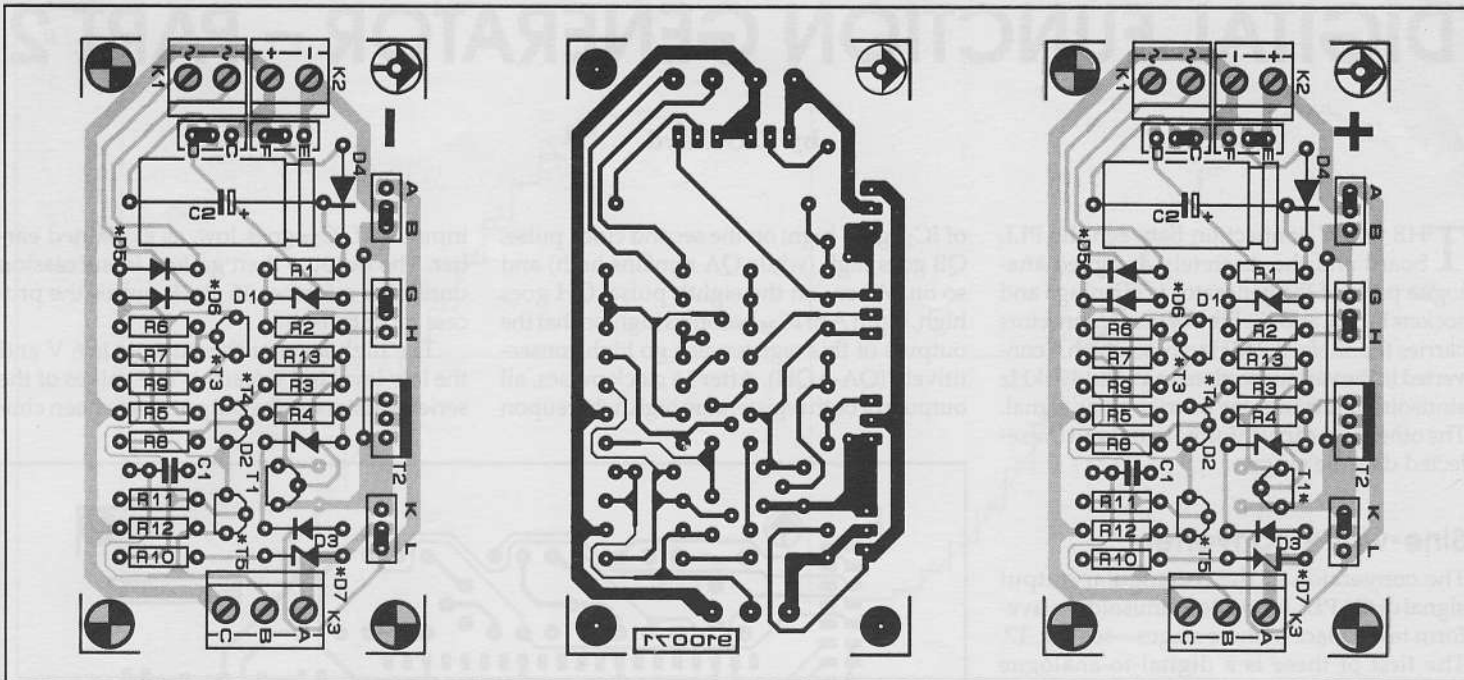


Fig. 4. Printed circuit boards are available for both versions of the dissipation limiter.

## PARTS LIST

### Resistors:

R1, R2 = 4.7 k $\Omega$   
 R3 = 100 k $\Omega$   
 R4 = 1 k $\Omega$   
 R5–9 = 22 k $\Omega$   
 R10, R11 = 220 k $\Omega$   
 R12 = 2.2 k $\Omega$   
 R13 = 100 k $\Omega$

### Capacitors:

C1 = 1 nF  
 C2 = 47  $\mu$ F, 100 V

### Semiconductors:

D1 = zener diode, 20 V, 400 mW  
 D2 = zener diode, 39 V, 400 mW  
 D3 = 1N4148  
 D4–6 = 1N4004  
 D7 = see text  
 T1, T3 = BC556B (pos); BC546B (neg)  
 T2 = BUZ10 or BUZ11 (see text)  
 T4, T5 = BC546B (pos); BC556B (neg)

### Miscellaneous:

Heat sink for T2  
 PCB 910071

## The practical circuit

The circuit in Fig. 3 may be split into the drive for the current switch, the switch itself ( $T_2$ ) and a 'thyristor'. The thyristor is formed by transistors  $T_3$  and  $T_5$ ; its cathode is connected to the output terminal of the series regulator.

The thyristor is switched on via zener diode  $D_7$  as soon as the voltage across the regulator exceeds the level fixed by the zener diode plus the b-e voltage of  $T_5$ . It switches itself off just before the next zero crossing. To make certain that it does, it is decoupled from the rectifier and the inverse diode of  $T_2$  via  $D_4$  and  $D_5$ , which are loaded by  $R_5$ .

When the thyristor is on,  $T_4$  switches  $T_1$  on and this in turn switches  $T_2$  off.

Transistor  $T_4$  also serves, in conjunction with  $R_3$ , to decouple the thyristor and the charging-current switch.

Diode  $D_4$  and  $C_2$  provide  $T_2$  with the necessary switching voltage.

Zener diode  $D_1$  protects the gate of  $T_2$  against overvoltage.

The inductance of the mains transformer causes a high back e.m.f. when the charging current is switched off, and this may upset the correct operation of  $T_2$ . This is prevented by  $D_2$  and  $D_3$ , which switch off  $T_2$  as soon as the back e.m.f. exceeds the permissible reverse bias. A useful effect of the back e.m.f. is that it increases the potential across  $C_2$ , which guarantees satisfactory switching of  $T_2$  even when the output voltage is a maximum.

Resistor  $R_{12}$  ensures correct switching of  $T_2$  when the output is not loaded (open circuit). It must be rated at  $U_{o(m)}^2/R_{12}$  Watt. It may be omitted if the power supply is permanently loaded.

Transistor  $T_2$  must be fitted, *insulated*, on its own heat sink or on that of the regulator.

Depending on the component values, the limiter may be used with secondary alternating voltages of up to 50 V<sub>peak</sub>. It is not possible to say what the maximum load current can be without knowing the value of the reservoir capacitor and the specification of the mains transformer. What can be said is that the maximum charging current pulses must not exceed the maximum permissible current through  $T_2$ , which is 19 A for the BUZ10 and 30 A for the BUZ11.

The limiter can be used without any problem in 5 A power supplies. The prototype operated satisfactorily with an output current of 10 A (reservoir capacitor was 10 000  $\mu$ F). It is always possible in doubtful cases to connect two or three SIPMOS transistors ( $T_2$ ) in parallel.

Here are some tips for calculating the val-

ues or ratings of a number of components.

- The zener voltage of  $D_7$  must be  $U_{so} - 0.7$  V ( $U_{b-e}$  of  $T_5$ ).
- The maximum reverse bias of  $T_2$  must be greater than the peak value of the potential across the reservoir capacitor.
- The zener voltage of  $D_2$  must be equal to the maximum reverse bias of  $T_2$  minus 5 V.
- Capacitor  $C_2$  must be rated at  $U_{so(m)}$  plus 20 V ( $D_1$ ).
- Transistor  $T_4$  must be able to withstand voltages of  $U_{so(m)}$  plus 20 V ( $D_1$ ).
- Transistors  $T_3$  and  $T_5$  must have a reverse bias rating equal to the peak value of the secondary alternating voltage.
- Resistor  $R_{12}$  must be rated at  $U_{o(m)}^2/R_{12}$  (watts).
- All connecting wires should be as short as possible and of appropriate thickness.
- The dimensions of the heat sink depend on the transformer, the reservoir capacitor and the maximum permissible short-circuit current.
- In most cases, it is possible to fit  $T_2$  on the heat sink of the regulator.

## Construction

The limiter described above is, of course, intended for positive voltages. One for negative voltages operates in a similar manner, but the polarity of some components must be reversed.

Whichever version is needed, it is best constructed on the appropriate printed-circuit board shown in Fig. 4. The differences between the two versions are indicated by an asterisk (\*).

It is recommended to 'strengthen' the broad tracks by soldering thick, bare wire on them.

The completed unit is, as shown in Fig. 3, interposed between the rectifier and the reservoir capacitor. Short, heavy-duty wiring should be used.